




**Department of Electrical
& Computer Engineering**
Faculty of Engineering & Architectural Science

Course Title:	Electronic Circuits I
Course Section:	ELE404
Semester/Year (e.g. F2017)	W2024

Instructor	Dr. Fei Yuan
-------------------	--------------

Assignment/Lab Number:	N/A
Assignment/Lab Title:	Design Project

Submission Date:	06/04/2024
Due Date:	06/04/2024, 23:59

Student LAST Name	Student FIRST Name	Student Number	Section	Signature*
Muruganantham	Haran	501166674	11	

*By signing above you attest that you have contributed to this written lab report and confirm that all work you have contributed to this lab report is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: <http://www.ryerson.ca/senate/current/pol60.pdf>

Table Of Contents

Circuit Description	2
Calculations	3
Simulations and Verification	4
Discrepancies/Notes	6
References	7

Circuit Description

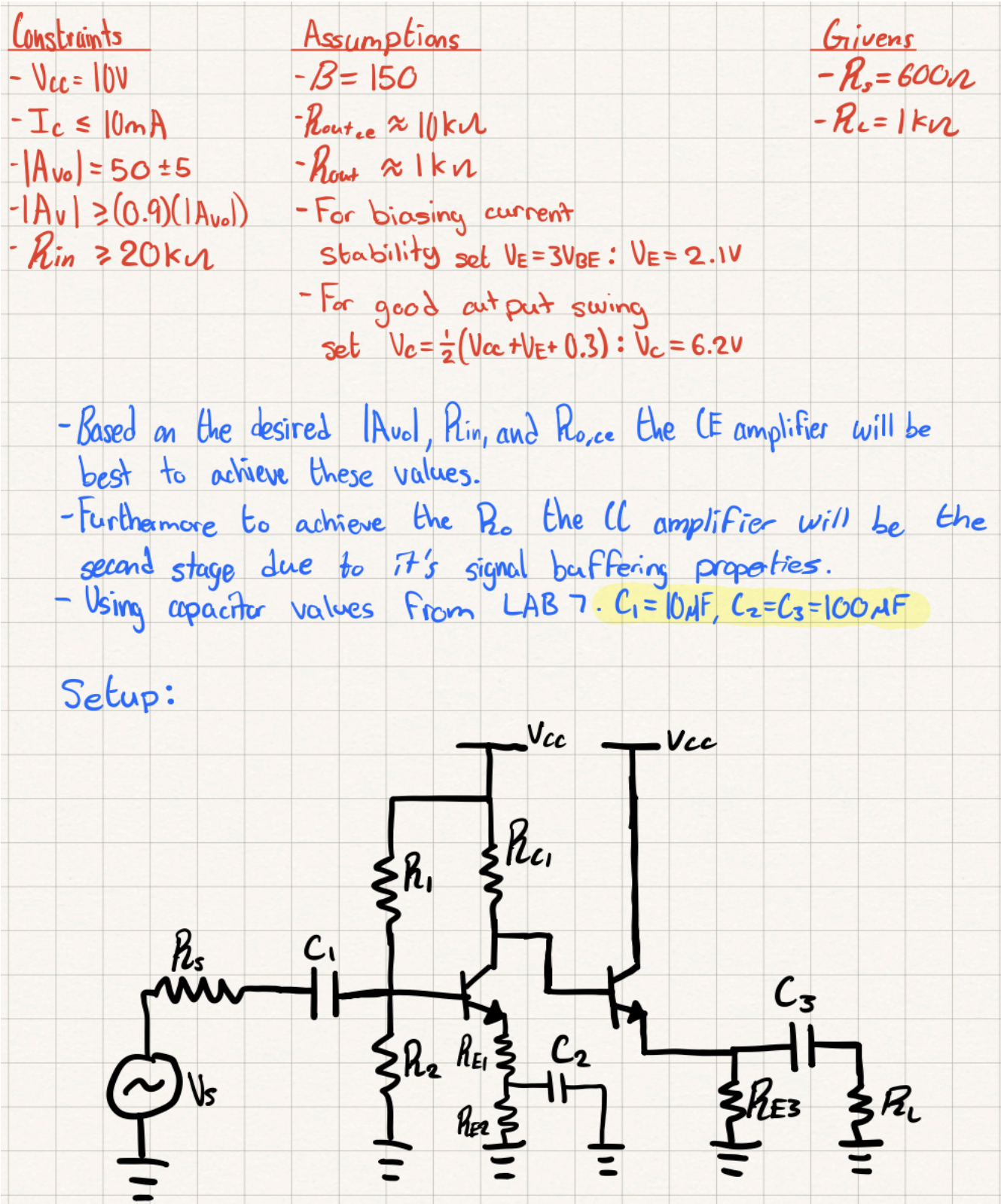


Figure 1. CE amplifier that cascades to a CC amplifier.

Calculations

$$I_c = \frac{V_{cc} - V_c}{R_c} \quad \text{- Since CE} \rightarrow R_{o,CE} \approx R_c = 10 \text{ k}\Omega$$

$$I_c = \frac{10 - 6.2}{10 \text{ k}} = 0.38 \text{ mA}$$

$$R_{E1} + R_{E2} = \frac{V_E}{I_E} = \frac{2.1 \text{ V}}{0.38 \text{ mA}} = 5.47 \text{ k}\Omega$$

$$I_c \approx I_E = 0.38 \text{ mA}$$

$$|A_{v0}| = \left| \frac{-g_m \cdot R_c}{1 + g_m \cdot R_{E1}} \right| = 50$$

$$g_m = 26 I_c \rightarrow g_m = 9.88 \text{ mS}$$

$$50 = \frac{(9.88)(10)}{1 + (9.88)(R_{E1})} \rightarrow R_{E1} = 0.0987 \text{ k}\Omega$$

$$R_{E2} = 5.37 \text{ k}\Omega$$

$$R_i \geq 20 \text{ k}\Omega$$

$$(R_1 \parallel R_2 \parallel R_i') \geq 20 \text{ k}\Omega$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_i'} \geq \frac{1}{20}$$

$$R_i' = r_{\pi} + (B+1) R_{E1}$$

$$R_i' = \frac{\beta}{g_m} + (B+1) R_{E1}$$

$$R_i' \approx 30 \text{ k}\Omega$$

$$R_1 \parallel R_2 \geq \left(\frac{1}{20} - \frac{1}{30} \right)^{-1}$$

$$R_1 \parallel R_2 \geq 60 \text{ k}\Omega$$

$$R_1 \parallel R_2 = 60 \text{ k}\Omega$$

$$V_B = V_{cc} \cdot \frac{R_2}{R_1 + R_2}$$

$$2.8 = 10 \cdot \frac{R_2}{R_1 + R_2}$$

$$\frac{R_1 \cdot R_2}{R_1 + R_2} = 60 \quad (1)$$

$$\frac{R_1 + R_2}{R_2} = 3.57 \quad (2)$$

$$\text{Solving eqn (1) \& (2)} \rightarrow R_1 = 214.2 \text{ k}\Omega$$

$$R_2 = 83.34 \text{ k}\Omega$$

$$R_o = R_{E3} \parallel R_{o,CE}$$

$$1 \text{ k}\Omega = \frac{R_{E3} \cdot (10 \text{ k}\Omega)}{R_{E3} + 10 \text{ k}\Omega} \rightarrow R_{E3} = 1.1 \text{ k}\Omega$$

Due to resistor constraints: $R_c = 10 \text{ k}\Omega$, $R_{E1} = 0.1 \text{ k}\Omega$, $R_{E2} = 5.6 \text{ k}\Omega$, $R_1 = 220 \text{ k}\Omega$,
and $R_2 = 82 \text{ k}\Omega$, $R_{E3} = 1.1 \text{ k}\Omega$

Simulations and Verification

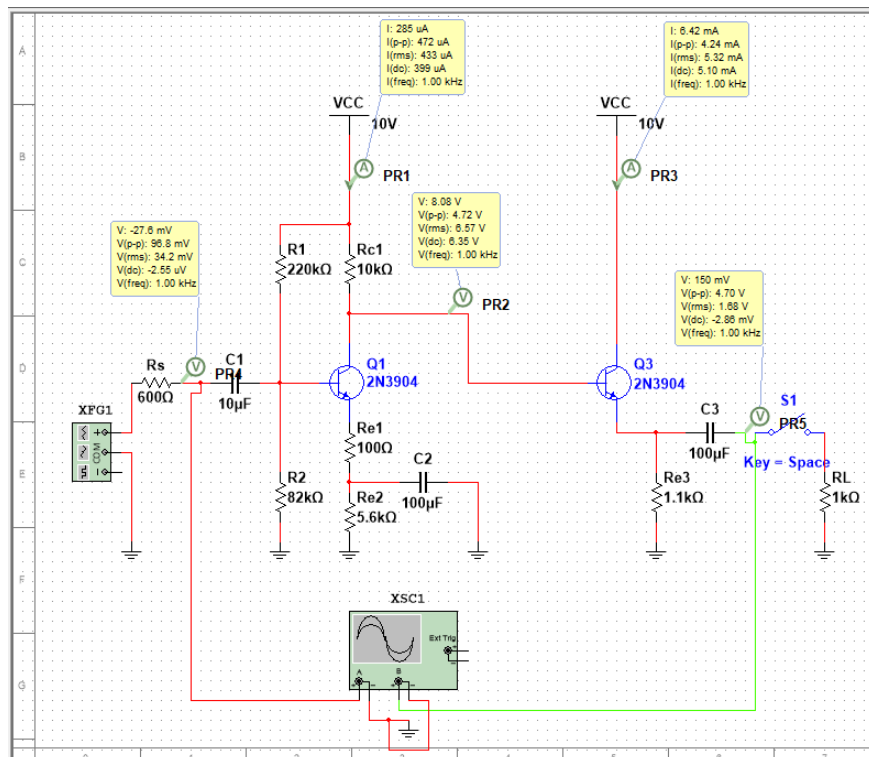


Figure 2. MultiSim simulation of amplifier with no load.

$$I_c = I_{c1} + I_{c2}$$

$$= 0.285 \text{ mA} + 6.42 \text{ mA}$$

$$= 6.705 \text{ mA} \leq 10 \text{ mA} \checkmark$$

$$|A_{v0}| = \frac{V_o}{V_i} = \frac{4.70}{0.0968} = 48.6$$

$$|A_{v0}| = 50 \pm 5 \rightarrow 45 \leq |A_{v0}| \leq 55$$

$$45 \leq 48.6 \leq 55 \checkmark$$

*Both values within spec *

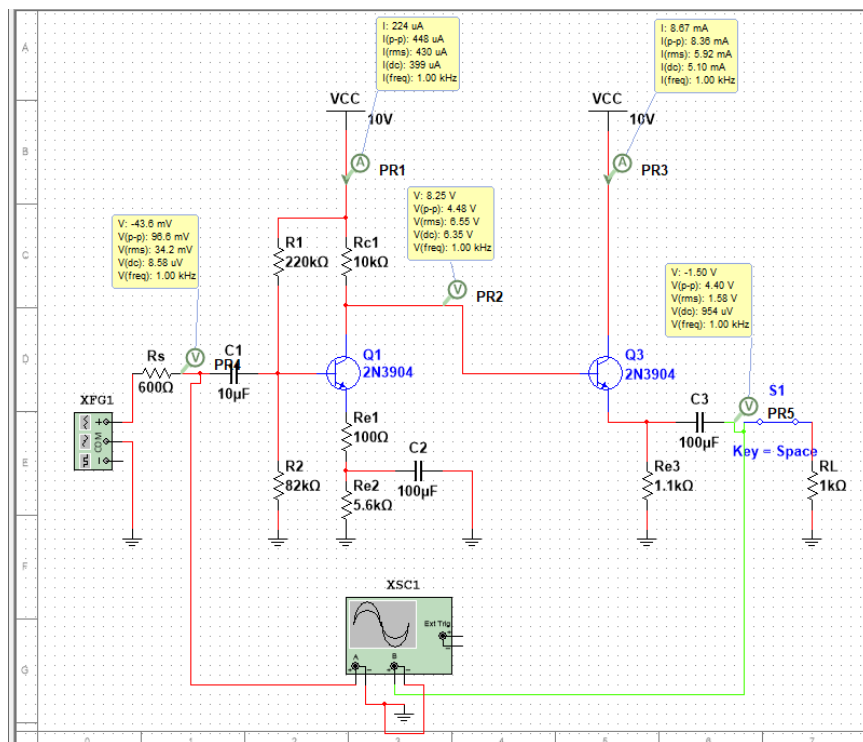


Figure 3. MultiSim simulation of amplifier with load.

$$I_c = I_{c1} + I_{c2}$$

$$= 0.224 \text{ mA} + 8.67 \text{ mA}$$

$$= 8.894 \text{ mA} \leq 10 \text{ mA} \checkmark$$


$$|A_v| = \frac{V_o}{V_i} = \frac{4.40}{0.0966} = 45.5$$

$$|A_{v0}|(0.9) = (48.6)(0.9)$$


$$= 43.7$$

$$45.5 \geq 43.7 \checkmark$$

*Both values within spec *

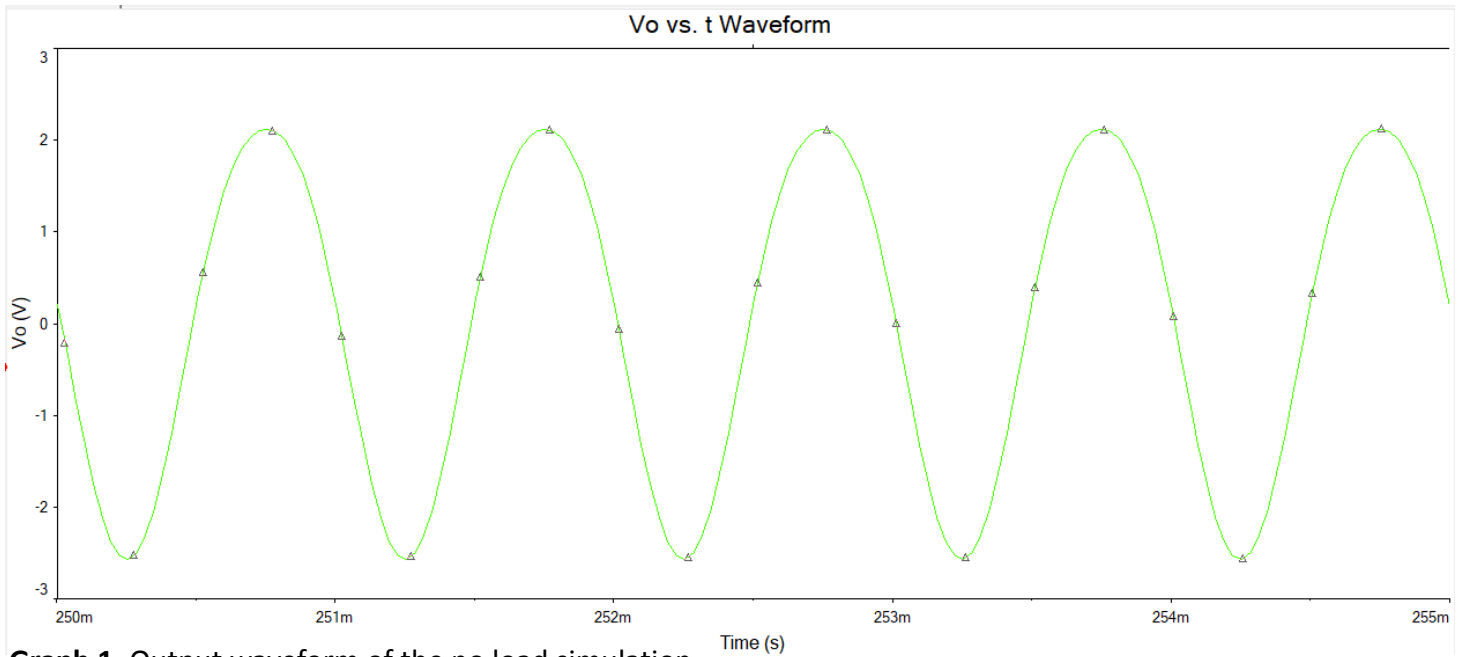

Graph 1. Output waveform of the no load simulation.

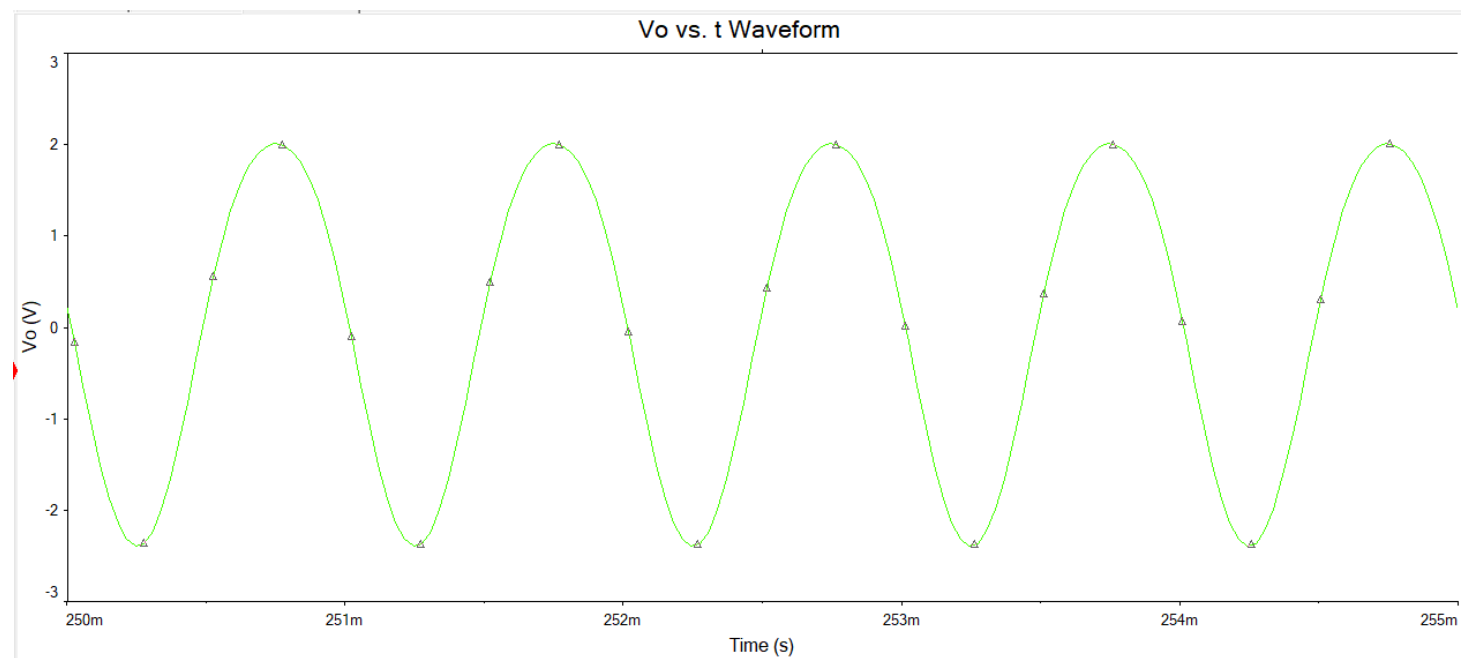

Graph 2. Output waveform of the loaded simulation.

Discrepancies/Notes

- The slight differences can most likely be attributed to the approximations made whilst doing initial calculations.
- Another reason for slight discrepancies was that whilst selecting the final resistance values, all of the values that were calculated had to be altered to meet the E24 constraints.

References

Lab 7 - Common-Collector (CC) Amplifier. (2024). Toronto Metropolitan University.

Yuan, Fei. (2024). *Module 3: BJT Voltage Amplifiers.* D2L Brightspace.

Kaler, Sandeep. (2023). *Lecture 9A.* Metropolitan Undergraduate Engineering Society